WELDON SCHOOL OF

BME 301: Bioelectricity BMI: Analog to Digital Converter

Please download the datasheet of your Analog-To-Digital (ADC) converter chip (http://www.analog.com/media/en/technical-documentation/data-sheets/16389fg.pdf) and answer the questions below relating to your ADC's specifications.

 Explain in your own words how Serial Peripheral Interface (SPI) allows the ADC chip to communicate with the Raspberry Pi (https://en.wikipedia.org/wiki/Serial_Peripheral_Interface)

The ADC onip takes an analog voltage and converts it into a digital signal that can be understood by the Rasberry Pi.
The SPI allows for this digital signal to be sent through the
MISO (Master Input Slave output). The Rasberry Pi, in this case being
the master, will send data to the ADC through the MOSI (master output
slave Input) and the CLK (serial clock), the latter determines the rate at which this communication happens

2. What is the dynamic / input voltage range of the ADC recalling that is powered from ground to 3.3V? The dynamic range of the ADC is equal to 3.3 v which is also the nighest voltage the ADC accepts.

3. What is the resolution of the ADC?


resolution =
$$\frac{\text{dynamic range}}{2^{\frac{1}{2}bits}} = \frac{3.3 \text{ v}}{2^{\frac{12}{2}}} = 0.000.806 \text{ v} = \boxed{0.806 \text{ mV}}$$

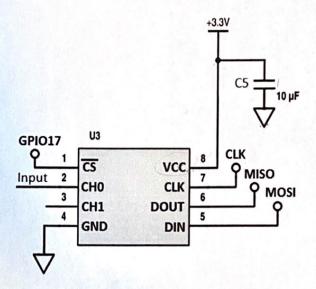4. How do you set the sampling frequency?

The CLK pin determines the rate at which the ADC measures the input analogue and communicates with the Rasherry Pi. This value is set by the "Master", in this care, the Rasherry Pi.



BME 301: Bioelectricity
BMI: Analog to Digital Converter



Using the schematic of the ADC, answer the below questions.

5. What is Cs for?
This corpacitor is used to prevent noise from entering the system by bypassing it to ground.

6. Why should C₅ be physically close the ADC on your circuit board?

The C₅ should physically be closer to the ADC on the circuit board to avoid noise.

Now build the ciruit above. Connect the GPIO17, CLK, MISO, MOSI to the plastic connector at the lower right portion of your board (now is a good time to solder in the appropriate connector). Submit a picture of your board, ensuring that the appropriate connections are visible and able to be followed.